

Capacitance

Background:

This chapter covers capacitance, and this chapter builds off of our understanding of electric charges and fields, Gauss's Law, and electric potential.

Major Topics:

The major topics covered in the capacitance unit are capacitance, capacitors in series, capacitors in parallel, energy in a capacitor, and dielectrics.


Important Vocabulary:

- Capacitance: a measure of a conductor's ability to store charge; units are Farads (F)
- Conventional Current: the movement of positive electron holes in a circuit
- Capacitors in Parallel: capacitors connected in a manner in which charges travel through either capacitor
- Capacitors in Series: capacitors connected in a manner in which charges travel through both capacitors
- Equivalent/Effective Capacitance: the overall capacitance of capacitors in parallel/series
- Dielectric: an insulator inserted between the plates of a capacitor; this insulator results in a decrease in the potential difference between the two plates by a factor K (dielectric constant)


Important formulae:

- $C = Q/V$
- Capacitors in Parallel: $C_{effective} = C_1 + C_2$
- Capacitors in Series: $\frac{1}{C_{effective}} = \frac{1}{C_1} + \frac{1}{C_2}$
- Energy in a Capacitor: $U = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} CV^2 = \frac{1}{2} QV$
- Dielectrics: $V = \frac{V_0}{K}$; $C = KC_0$
- Parallel Plate Capacitors with a Dielectric: $C_{||} = K \frac{A\epsilon_0}{d}$


Diagrams:

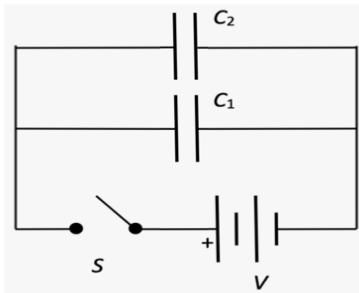

Capacitors in Parallel

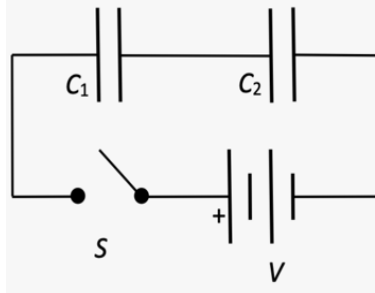

Capacitors in Series

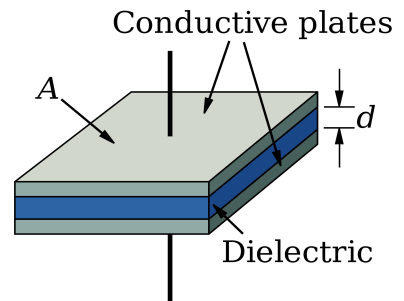

Dielectric

Capacitance

- 1) Calculate the voltage applied to a $2.00\mu\text{F}$ capacitor when it holds $3.10\mu\text{C}$ of charge.

Solution

This is just a manipulation of our general equation, $C = Q/V$

$$C = Q/V$$


$$V = Q/C$$

$$V = (3.10 \times 10^{-6}) / (2.00 \times 10^{-6})$$

$$V = \boxed{1.55\text{V}}$$

Capacitance

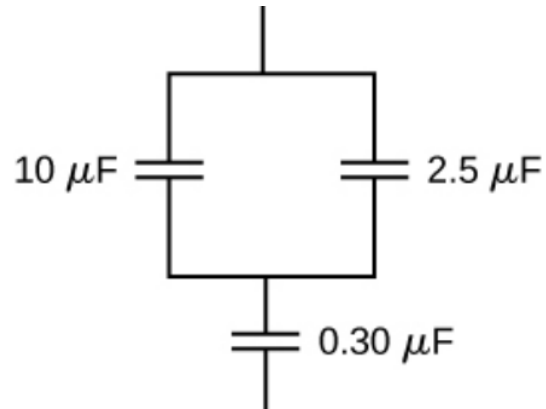- 2) Find the total capacitance of this combination of series and parallel capacitors shown to the right.



Solution

The first step is to find C_{eq} of the capacitors in parallel.

$$C_{eq_1} = C_1 + C_2$$

$$C_{eq_1} = (2.5e-6) + (10e-6)$$

$$C_{eq_1} = 1.25e-5\text{ F}$$

Using C_{eq_1} , find C_{eq} of the whole system by treating it as capacitors in series.

$$\frac{1}{C_{eq_2}} = \frac{1}{C_{eq_1}} + \frac{1}{C_3}$$

$$\frac{1}{C_{eq_2}} = \frac{1}{1.25e-5} + \frac{1}{0.30e-6}$$

$$\frac{1}{C_{eq_2}} = 3413333.333$$


$$C_{eq_2} = \frac{1}{3413333.333}$$

$$C_{eq_2} = \boxed{2.93e-7\text{ F}}$$

Capacitance

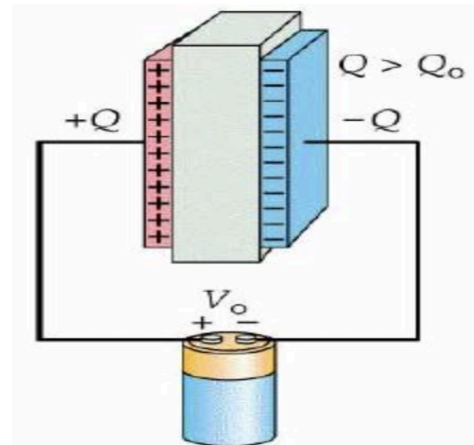- 3) Let's say there is a parallel plate capacitor with the battery connected. Given that the battery stays connected while a dielectric is inserted, determine if the following quantities will increase, decrease, or stay the same.

- Potential difference (V)
- Capacitance (C)
- Charge (Q)
- Electric Field (E)
- Energy (U)



Solution

- Since the battery is connected, V stays the same.
- C will increase, given by $C = KC_0$, which means that C increases by a factor K , the dielectric constant.
- Using $Q = CV$, since C increases and V stays the same, Q must increase as well.
- Using $V = Ed$, since V and d remain constant, E also stays the same.
- Using $U = \frac{1}{2}QV$, since Q increases and V stays the same, U must increase as well.